



॥ त्वं ज्ञानमयो विज्ञानमयोऽसि ॥


COMPUTER ARCHITECTURE

CSL3020

Deepak Mishra

<http://home.iitj.ac.in/~dmishra/>
Department of Computer Science and Engineering
Indian Institute of Technology Jodhpur


An abstract view

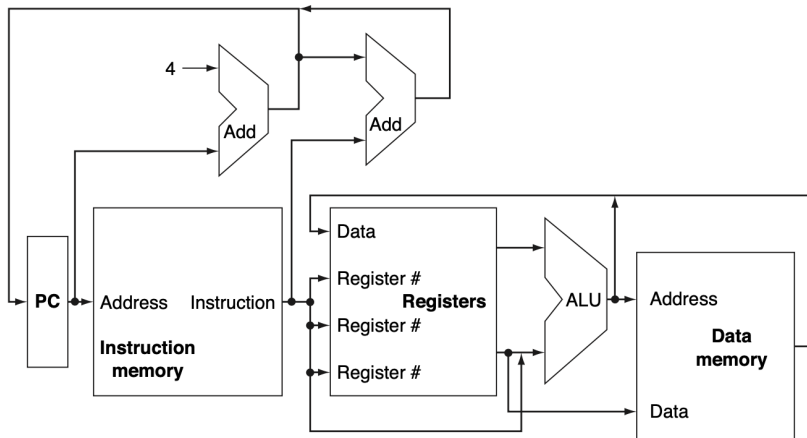

An abstract view

- All instructions start by using the PC to supply instruction address.
- After the instruction is fetched, the register operands are specified.
- Operands then can be operated on to compute a memory address, an arithmetic result, or a comparison.
- The result from ALU or memory is written back into the register file.
- Branches use ALU to determine the next instruction address.
- The thick lines interconnecting the functional units represent buses, which consist of multiple signals.

A Simple MIPS Processor

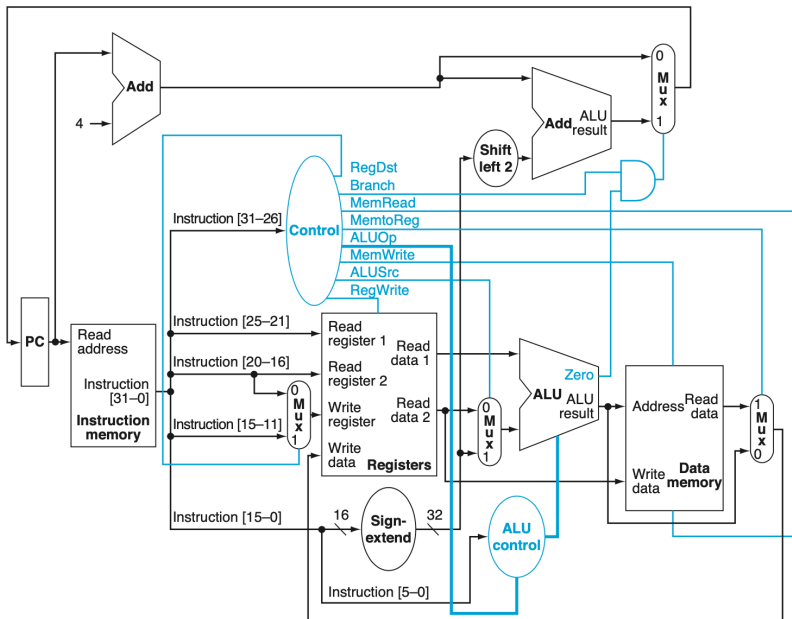

Functional Units

Two types of functional units:

- *Combinational*: Elements that operate on data values; output is function of current input only
- *Sequential*: Elements that contain state (memory); output is function of current and previous inputs


Functional Units

Two types of functional units:

- *Combinational*: Elements that operate on data values; output is function of current input only
- *Sequential*: Elements that contain state (memory); output is function of current and previous inputs


Clocked and timing

 - Clocking methodology defines when signals can be read and written
- We will assume an edge-triggered clocking methodology.




A Simple MIPS Processor - RF

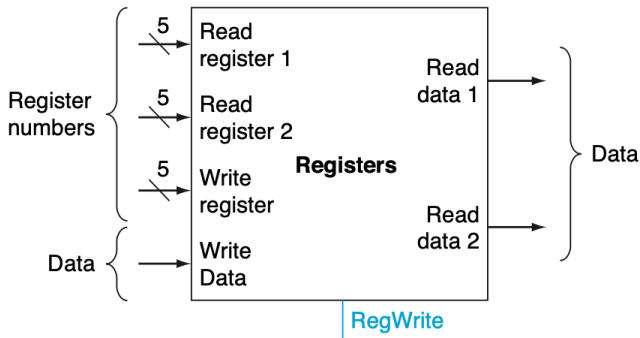- The RF (register file) contains all the registers and has two read ports and one write port.
- A register write must be explicitly indicated by asserting the write control signal.




A Simple MIPS Processor - ALU

 - Operation to be performed by the ALU is controlled with the ALU operation signal.
- Zero detection output is used to implement branches.



A Simple MIPS Processor - Memories

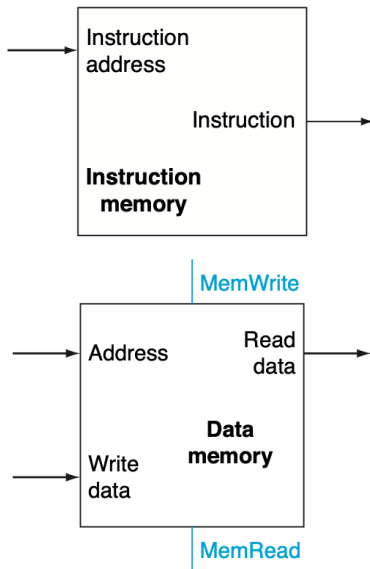
- We assume that the instruction memory need to provide only read access because the datapath does not write instructions.
- In contrast, the data memory needs to provide both read and write access with control signals.



A Simple MIPS Processor - MIPS ISA Subset

- Arithmetic - logic instructions
 - add, sub, AND, OR, slt
- Memory reference instructions
 - lw, sw
- Branching instructions
 - beq, j

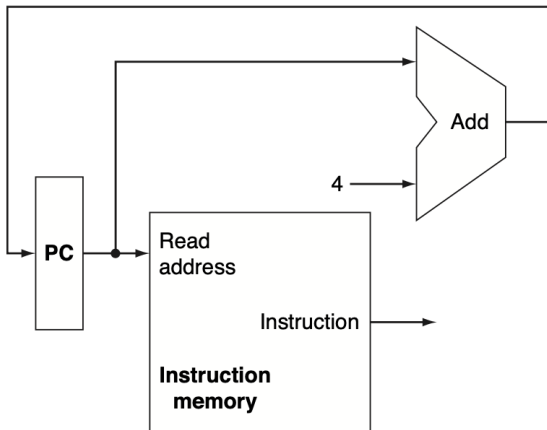
A Simple MIPS Processor - Instruction Fetch



Implementing R-type and memory instructions

- Arithmetic and logical instructions use ALU with the inputs coming from the two registers.
- Memory instructions also use ALU for address calculation using sign-extended 16-bit offset.
- The value stored into a destination register comes from ALU (for an R-type instruction) or memory (for a load).

A Simple MIPS Processor - R-type

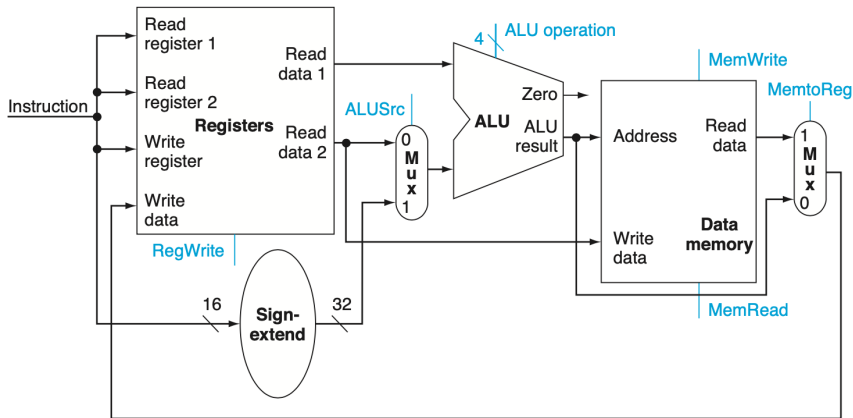


Implementing branch instruction (beq)

- The branch datapath must do two operations – compute the branch target address and compare the register contents.
- It needs an ALU to evaluate the branch condition and a separate adder to compute the branch target as the sum of the incremented PC and the sign-extended offset.
- In sign extension, the lower 16 bits of the instruction are first extended to 32 bits and then shifted left 2 bits for word alignment.


A Simple MIPS Processor - Branching

Putting it all together

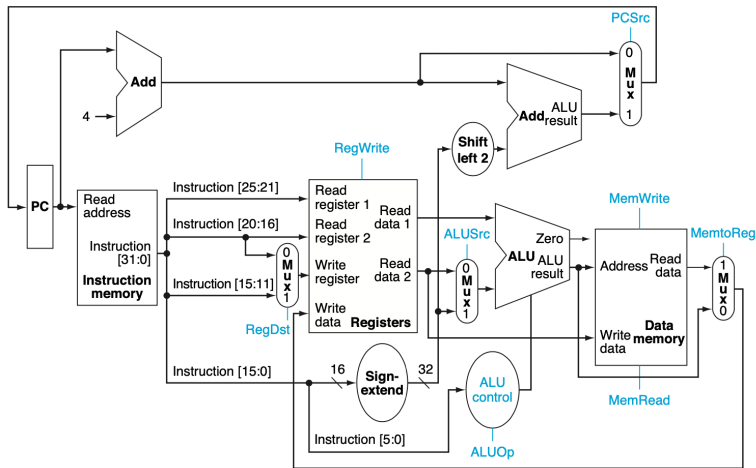

A Simple MIPS Processor

Putting it all together with control

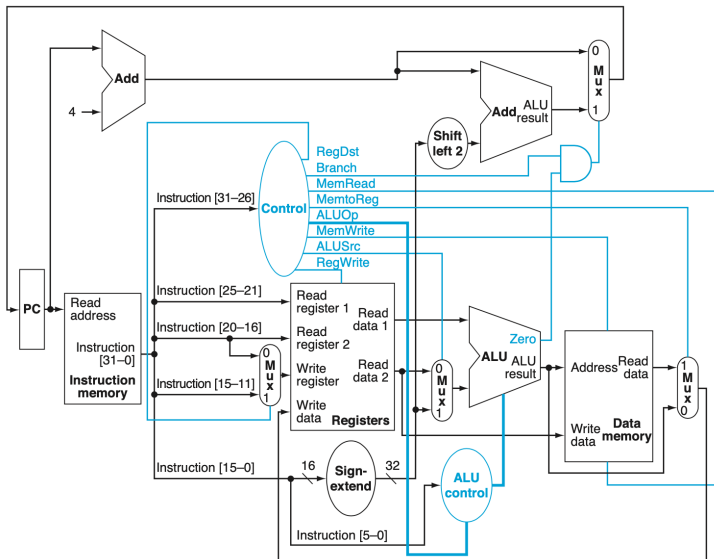


Extending to include the jump instruction

- We can implement a jump by storing into the PC the concatenation of
 - the upper 4 bits of the current PC + 4 (these are bits 31:28 of the sequentially following instruction address)
 - the 26-bit immediate field of the jump instruction
 - the bits 00
- An additional multiplexer is required to choose between the jump target and the branch target.

A Simple MIPS Processor - Jump

Including the jump instruction

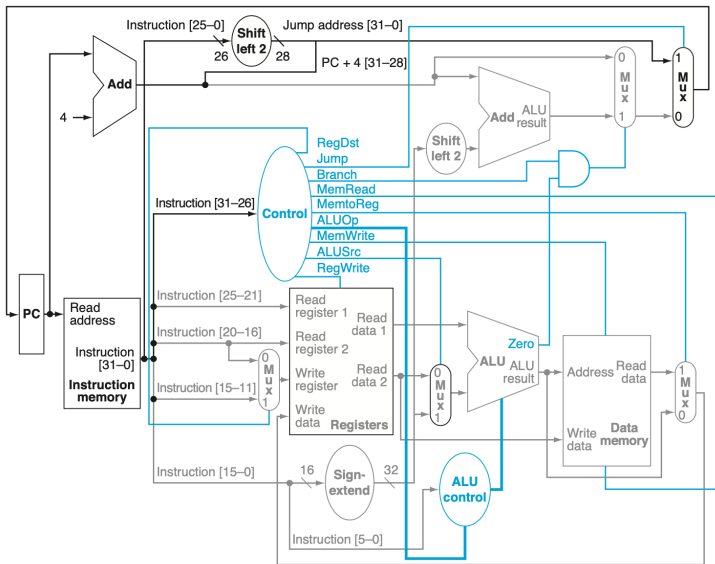


A Simple MIPS Processor - Control

Instru ction	Opcode	RegDst	RegWrite	ALUsrc	MemWrite	MemRead	MemtoReg	Branch	Jump
Rtype	000000	1	1	0	0	0	0	0	0
Sw	101011	X	0	1	1	0	X	0	0
Lw	100011	0	1	1	0	1	1	0	0
Beq	000100	X	0	0	0	0	X	1	0
J	000010	X	0	X	0	0	X	X	1

A Simple MIPS Processor - Control

Instruction	Opcode	RegDst	RegWrite	ALUSrc	MemWrite	MemRead	MemtoReg	Branch	Jump
Rtype	000000	1	1	0	0	0	0	0	0
Sw	101011	X	0	1	1	0	X	0	0
Lw	100011	0	1	1	0	1	1	0	0
Beq	000100	X	0	0	0	0	X	1	0
J	000010	X	0	X	0	0	X	X	1

Inputs

 

Hardwired vs. Microprogrammed Control

Hardwired	Microprogrammed
Generates control signals using logic circuits	Generates control signals using micro instructions stored in control memory
Faster and costlier	Slower but less costly
Difficult to modify	Easy to modify as the modification need to be done only at the instruction level
Used in RISC, cannot handle complex instructions	Used in CISC

A few comments on control

- Controls are set using 6-bit opcode field, op ([31:26]), of instruction.
- It is easy to control the operation while using single-cycle implementation.
- However single-cycle design is inefficient as the clock cycle is determined by the longest possible path in the processor.
- Although the CPI is 1, the overall performance of a single-cycle implementation is poor, since the clock cycle is too long.
- An alternative is Pipelining.